



# FPGA Lab-05

---

Keyboard(1)




# Lab Content

---

- Using the keyboard as input tool, the keyed-in numbers from 0 to 9 are indicated by 10 different LEDs.
- Lab 1: Keyboard Detection Circuitry
- Lab 2 : Keyboard Buffer
- Lab 3: BCD code to LED output circuitry.

# System Block Diagram

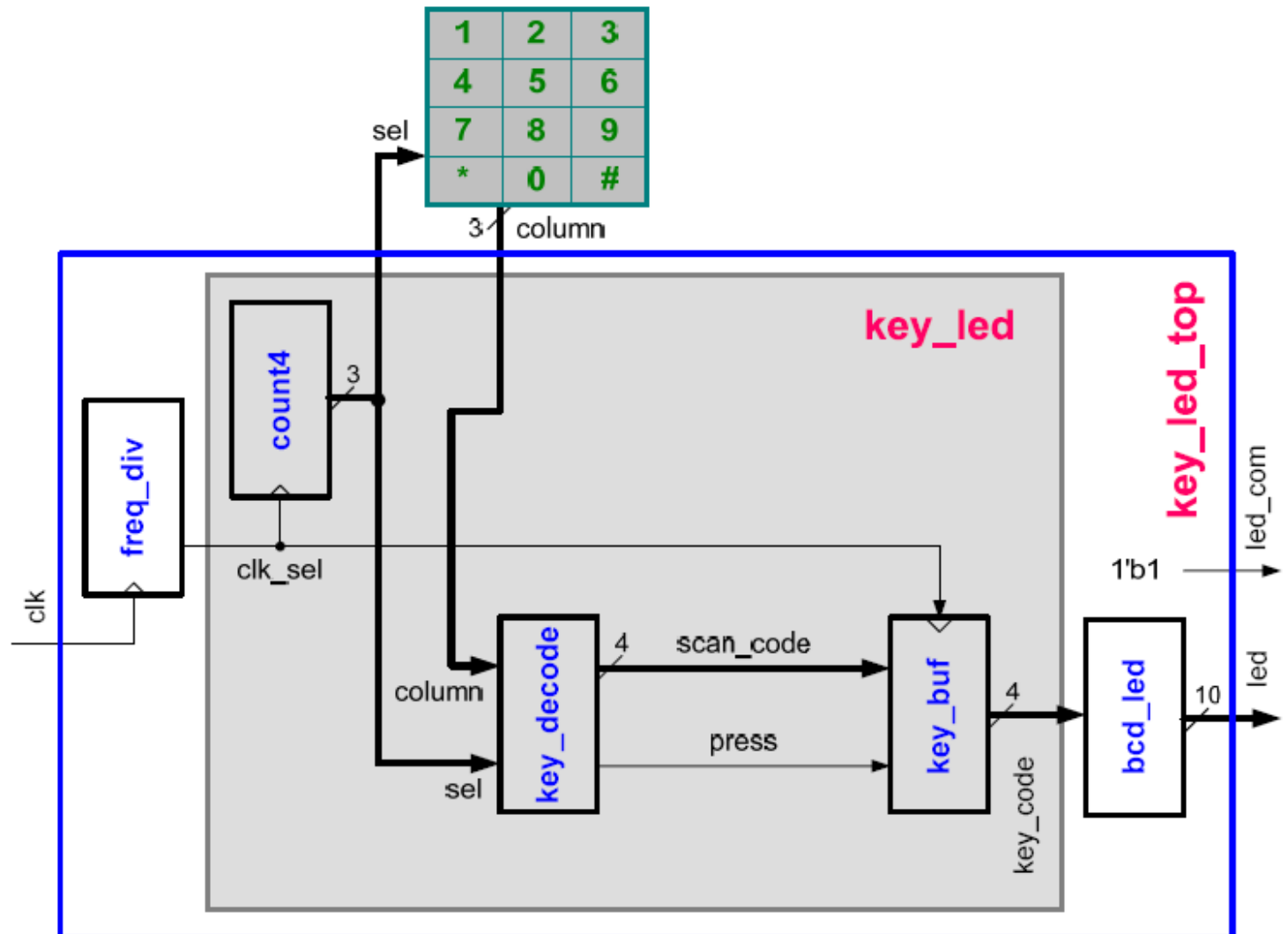




# Verilog Codes

---

- key\_decode.v
- key\_buf.v
- key\_led.v
- key\_led\_top.v
- bcd\_led.v
- count4.v (Please write it yourself)
- freq\_div.v(Please write it yourself)
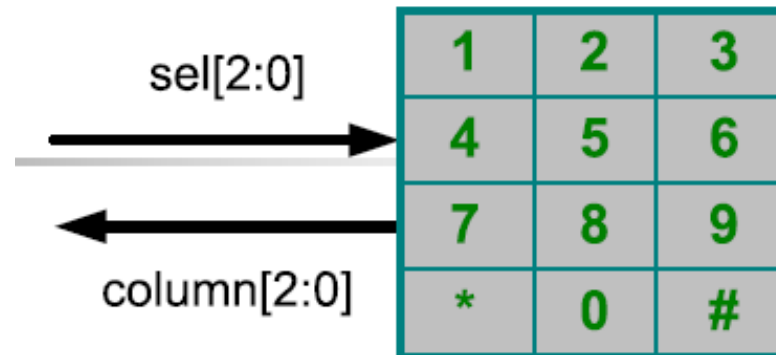
# How the keyboard works


- When sel= 000, if column = 011, it means the code typed is 1 (0001).
- When sel= 000, If column = 101, then the code entered is 2 (0010).
- When sel= 000, If column = 110, then the keyed-in code is 3 (0011)
- When sel= 001, If column = 011, then the keyed-in code is 4 (0100)
- When sel= 001, If column = 101, then the keyed-in code is 5 (0101)
- When sel= 001, If column = 110, then the keyed-in code is 6 (0110)
- When sel= 010, if column = 011, then the keyed-in code is 7 (0111)
- When sel= 010, If column = 101, then the keyed-in code is 8 (1000)
- when sel= 010, If column = 110, then the keyed-in code is 9 (1001)
- When sel= 011, if column = 101, then the keyed-in code is 0 (0000).


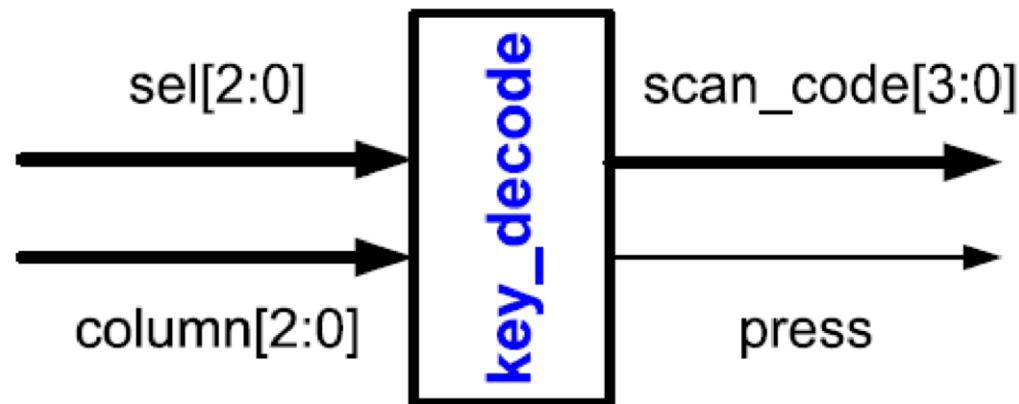
## Step 1: Keyboard detection circuit

---

- The input signal (`sel[2:0]`) and the input signal (`column[2:0]`) of the keyboard are used to determine whether a number is keyed in or not (determined by `press`).
- If there is a keyed-in number (`press` is 1), the BCD code (`scan_code[3:0]`) of the keyed-in number is generated



# VerilogCode -key\_decode.v(1/3)

---

- module key\_decode(sel, column, press, scan\_code);
- input[2:0]sel;
- input[2:0] column;
- output press;
- output[3:0] scan\_code;
- reg[3:0] scan\_code;
- reg press;
- always@(sel or column) begin
- case(sel)

# VerilogCode -key\_decode.v(2/3)

---

- 3'b000:
- case(column)
- 3'b011: begin scan\_code= 4'b0001; press = 1'b1; end // 1
- 3'b101: begin scan\_code= 4'b0010; press = 1'b1; end // 2
- 3'b110: begin scan\_code= 4'b0011; press = 1'b1; end // 3
- default: begin scan\_code= 4'b1111; press = 1'b0; end
- endcase
- 3'b001:
- case(column)
- ~~your code~~~
- endcase
- 3'b010:
- case(column)
- ~~your code~~~
- endcase




# VerilogCode -key\_decode.v(3/3)

---

- 3'b011:
- case(column)
- `~~your code~~~`
- endcase
- default:
- begin scan\_code= 4'b1111; press = 1'b0; end
- endcase
- end
- endmodule

## Step 2: Keyboard Buffer

---

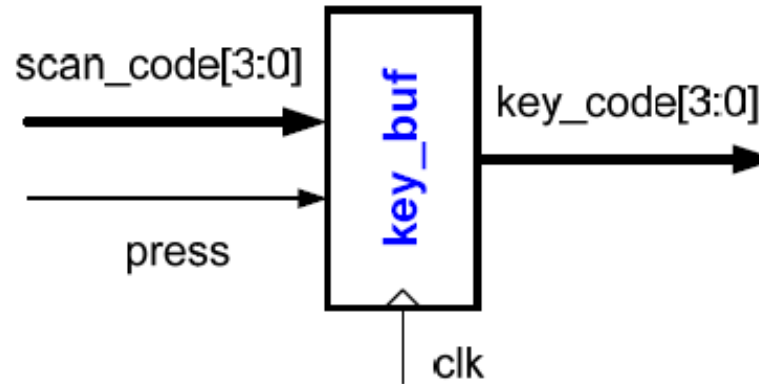

- Store the number typed by the keyboard. Whenever clk is triggered,
- If press is 1, it means there is a number typed on the keyboard (scan\_code[3:0]). The scan\_code will be stored in key\_code[3:0].
- If press is 0 when clk is triggered, it means there is no number typed on the keyboard, and the content of key\_code remains unchanged.

# VerilogCode -key\_buf.v

---

- module key\_buf(clk, rst, press, scan\_code, key\_code);
- input clk, rst, press;
- input[3:0] scan\_code;
- output[3:0]key\_code;
- reg[3:0]key\_code;
- always@(posedge clk or posedge rst) begin
- if(rst)
- key\_code= 4'b1111;// initial value
- else
- key\_code= press ? ~~your code~~~;
- end
- endmodule



## Lab 3: BCD code to LED output circuitry.

---

- bcd\_led.v
- key\_led.v
- key\_led\_top.v

# bcd\_led.v

---

- module bcd\_led(key\_code, led);
- input[3:0]key\_code;
- output[9:0]led;
- reg[9:0]led;
- always@(key\_code) begin
- case(key\_code)
- 4'b0000: led = 10'b0000000001; //0 to 9的LED display
- ~~your code~~
- default: led = 10'b0000000000;
- endcase
- end
- endmodule

# key\_led

---

- module key\_led(clk\_sel, reset, column, sel, key\_code);
- input clk\_sel, reset;
- input[2:0]column;
- output[2:0]sel;
- output[3:0] key\_code;
- wire press;
- wire[3:0] scan\_code, key\_code;
- count4(~~your code~~~ );
- key\_decode(~~your code~~~);
- key\_buf(~~your code~~~);
- endmodule

# key\_led\_top.v

---

- module key\_led\_top(clk, reset, column, sel, led, led\_com);
- input clk, reset;     //pinW16,C16
- input[2:0]column;     // pin AA13, AB12, Y16
- output[2:0]sel;     // pin AB10, AB11, AA12
- output[9:0]led;     // pin E2, D3, C2, C1 ,L2, L1, G2, G1, U2, N1
- output led\_com;     // pin N20
- assign led\_com= 1'b1;
- wire clk\_sel;
- wire[3:0] key\_code;
- freq\_div#(13) (~~your code~~ );
- key\_led(~~your code~~ );
- bcd\_led(~~your code~~ );
- endmodule