



FPGA Lab-07

Red and green light control circuit


實驗內容

- Design a daytime and nighttime traffic light control circuit.
- **Daytime (Mode 0~5 repeat cycle):**
- Mode = 0, Green 1 is on, Red 2 is on (20 sec.)
- Mode = 1, Green 1 flashing, Red 2 on (5 seconds)
- Mode = 2, Yellow 1 is on, Red 2 is on (4 seconds)
- Mode = 3, Red 1 on, Green 2 on (after 20 seconds)
- Mode = 4, Red 1 is on, Green 2 is flashing (after 5 seconds)
- **Night :**
- Yellow light 1 blinking, yellow light 2 blinking
- 7-segment display counts down the red light at the same time as the green light sign.
- 7-segment display 0 at night


Verilog Codes

- light_cnt_dn_29.v (countdown 29~0)
- ryg_ctl.v (Control Mode 0~5 repeatedly)
- traffic.v (Combine light_cnt_dn_29. and ryg_ctl.v)
- traffic_top.v (Combine all the module)
- freq_div.v (straight use from previous code)
- seg7_select.v (straight use from previous code)
- bcd_to_seg7.v (straight use from previous code)

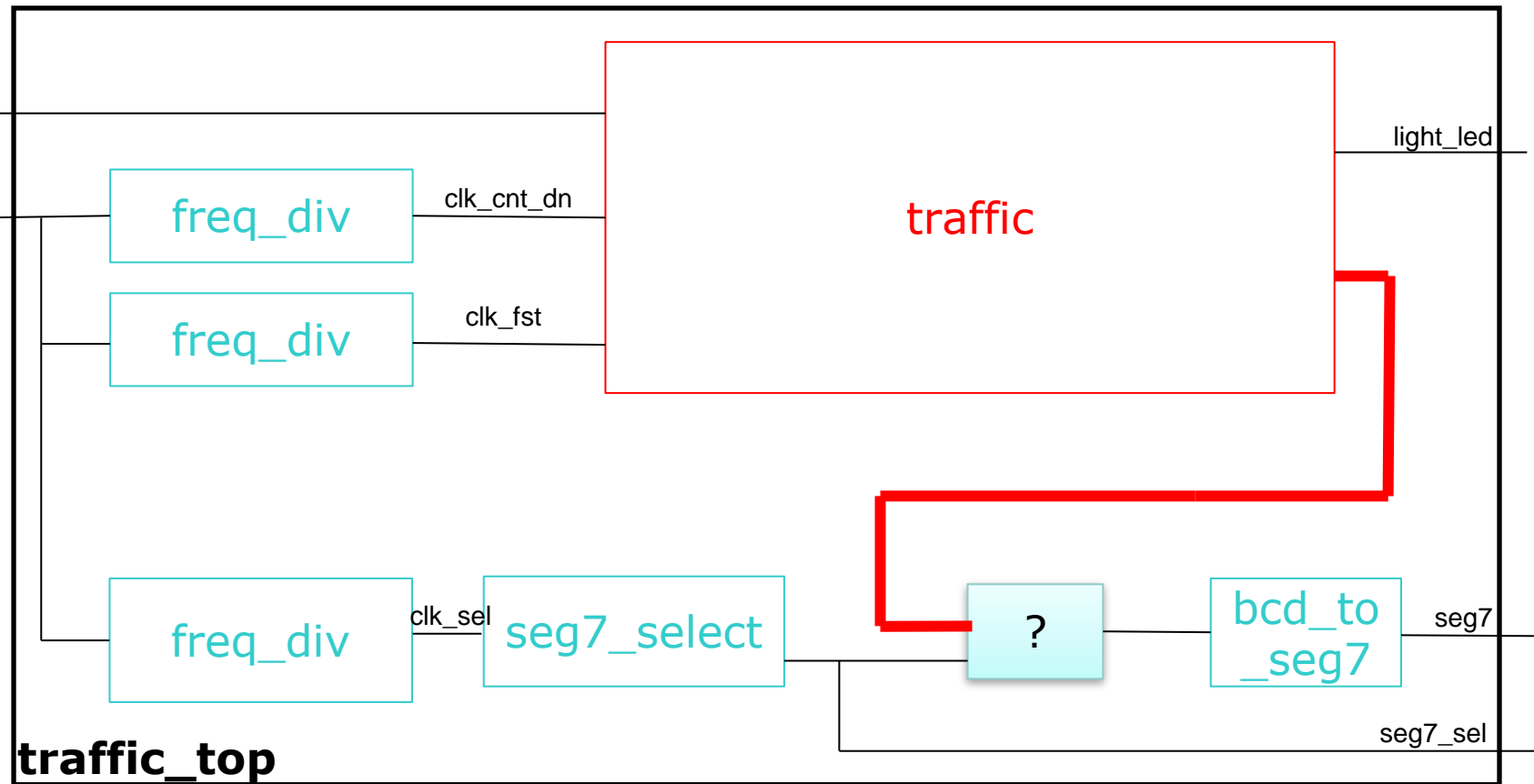Program Architecture (1/3) **traffic_top.v**



Program Architecture (2/3) **traffic.v**

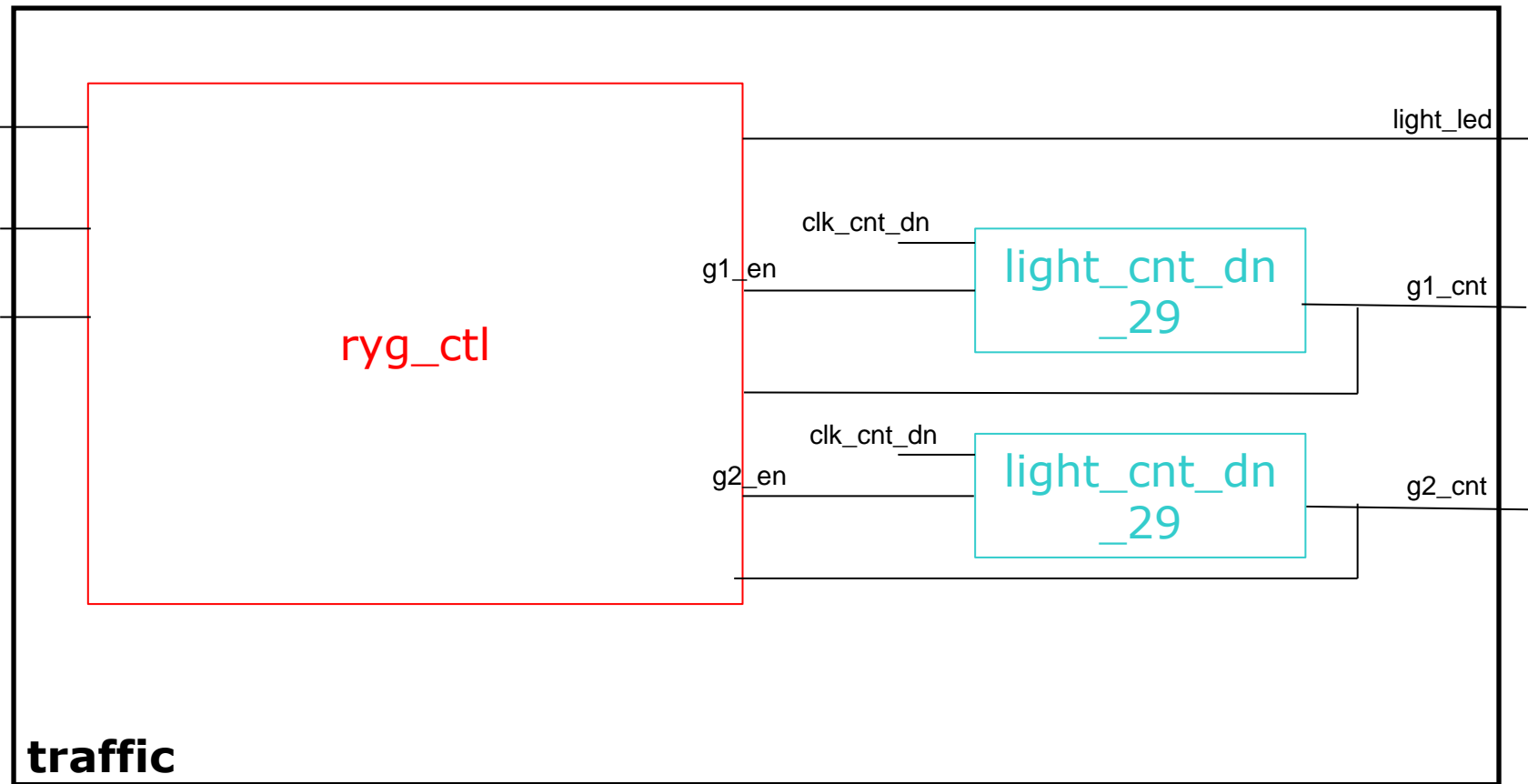

?

Tip: Generate control signals within your stage.

Program Architecture (3/3)

How to make data selections

- : of the seven-segment display position
- Console control signals
- Grabbing clues for stage switching points
- Adding a new control signal







light_cnt_dn_29.v

```
○ module light_cnt_dn_29 (clk, rst, enable, cnt);
○   input          clk, rst, enable;
○   output[7:0]    cnt;
○   reg[7:0]       cnt; //MSB[7:4] for tens digits, LSB [3:0] for ones digits
○   always@(posedge clk or posedge rst) begin
○     if(rst)
○       cnt= 8'b0; // initial state
○     else if(enable) // 0 -> 29 -> 24 -> ... -> 1 -> 0 -> 29
○       if(cnt== 8'b0)
○         your code; // 29
○       else if(cnt[3:0] == 4'd0) begin // 20 -> 19, 10 -> 09
○         your code;
○         your code;
○       end
○     else
○       your code; // 19 -> 18, 18 -> 17, 17 -> 16, ...
○   else cnt=8'b0;
○   end
○ endmodule
```

ryg_ctl.v(1/5)


- module **ryg_ctl** (clk_fst, clk_cnt_dn, rst, day_night, g1_cnt, g2_cnt, g1_en, g2_en, light_led);
- input clk_fst, clk_cnt_dn, rst, day_night;
- input[7:0] g1_cnt, g2_cnt;
- output g1_en, g2_en;
- output[5:0] light_led;
- reg g1_en, g2_en;
- reg[5:0] light_led;
- reg[2:0] mode;

ryg_ctl.v(2/5)

- always@(posedge clk_fst or posedge rst) begin
- if (rst)begin
- light_led <= 6'b001_100; // g1 : r2  
- mode <= 3'b0;
- g1_en <= 1'b0;
- g2_en <= 1'b0;
- end
- else if(day_night == 1'b1) // day time
- case(mode)
- 3'd0: begin
- light_led <= 6'b001_100; // g1 : r2  
- g1_en <= 1'b1; // g1 count down
- if(g1_cnt == 8'b0000_1001) // after 20 seconds
- mode <= mode + 3'b1;
- end


ryg_ctl.v(3/5)

```
○ 3'd1: begin    // g1 flashes : r2
○               if (g1_cnt == 8'b0000_0100) //after 5 seconds
○               mode <= mode + 3'b1;
○               else
○               light_led[3] <= clk_cnt_dn; // g1 flashes
○               end
○ 3'd2: begin
○               light_led = 6'b010_100;    // y1 : r2
○               if (g1_cnt == 8'b0000_0000) begin // after 4 seconds
○               g1_en <= 1'b0;
○               mode <= mode + 3'b1;
○               end
○               end
```

 

ryg_ctl.v(4/5)
 
```
○ 3'd3: begin
○     light_led <= 6'b100_001; // r1 : g2
○     g2_en <= 1'b1;
○     if(g2_cnt == 8'b0000_1001) // after 20 seconds
○         mode <= mode + 3'b1;
○     end
○ 3'd4: begin // r1 : g2 flashes
○     if(g2_cnt == 8'b0000_0100) // after 5 seconds
○         mode <= mode + 3'b1;
○     else
○         light_led[0] <= clk_cnt_dn; // g2 flashes
○     end
```





ryg_ctl.v(5/5)

```

○ 3'd5: begin
○   light_led <= 6'b100_010;           // r1 : y2
○   if (g2_cnt == 8'b0000_0000) begin // after 4 seconds
○     g2_en <= 1'b0;
○     mode <= 3'b0;
○   end
○   end
○ default: begin // back to mode0
○   light_led <= 6'b001_100;           // g1 : r2
○   g1_en <= 1'b1; // g1 count down
○   if(g1_cnt == 8'b0000_1001)         // after 20 seconds
○     mode <= mode + 3'b1;
○   end
○ endcase
○ else if(day_night == 1'b0)begin // night time
○   row_en <= 2'b11;
○   light_led <= {{1'b0, clk_cnt_dn, 1'b0}, {1'b0, clk_cnt_dn, 1'b0}};
○   // y1 flashes : y2 flashes
○   g1_en <= 1'b0;
○   g2_en <= 1'b0;
○   end
○ end
○ endmodule

```

  

traffic.v

- module **traffic** (clk_fst, clk_cnt_dn, rst, day_night, g1_cnt, g2_cnt, light_led);
- input clk_fst, clk_cnt_dn, rst, day_night;
- output[5:0] light_led;
- output[7:0] g1_cnt;
- output[7:0] g2_cnt;
- wire g1_en, g2_en;
- wire[7:0] g1_cnt;
- wire[7:0] g2_cnt;
- ryg_ctl M0(your code);
- light_cnt_dn_29 M1(your code); // for light 1
- light_cnt_dn_29 M2(your code); // for light 2
- endmodule

traffic_top.v(1/2)

- module **traffic_top**(clk, rst, day_night, light_led, led_com, seg7_out, seg7_sel);
- Input clk;
- Input rst;
- input day_night;
- output[5:0] light_led;//pin E2 ,D3 ,C2 ,N1 ,AA1 ,AA1\2
- output led_com;//pin N20
- output[2:0] seg7_sel;//pin AB10 ,AB11, AA12
- output[6:0] seg7_out;
- wire led_com;
- wire clk_cnt_dn;
- wire[7:0] g1_cnt;
- wire[7:0] g2_cnt;
- wire[3:0] count_out;

traffic_top.v(2/2)

- assign led_com= 1'b1;
- assign count_out = your code;
- freq_div#(23) M0(clk, rst, clk_cnt_dn);
- freq_div#(21) M1(clk, rst, clk_fst);
- freq_div#(15) M2(clk, rst, clk_sel);
- traffic M3(your code);
- bcd_to_seg7 M4(your code);
- seg7_select#(?) M5(your code);
- endmodule



Extra Question

- Creating pedestrian signals in the LED matrix:
- 20 seconds before the green light countdown: Green Man walking
- 5 seconds left of green countdown: Green man running
- Yellow light: Little Red Man
- Red light: Little Red Man