




FPGA Lab-03


Application of seven-segment displays(2)--- Display a 24 hours clock

Lab

 - Lab 1 : Design a counter from 00 to 59 ◦
- Lab 2 : Design a counter from 00-23 BCD Counter ◦
- Lab 3 : Design a 24 hours timer on display ◦




Architecture model for clock

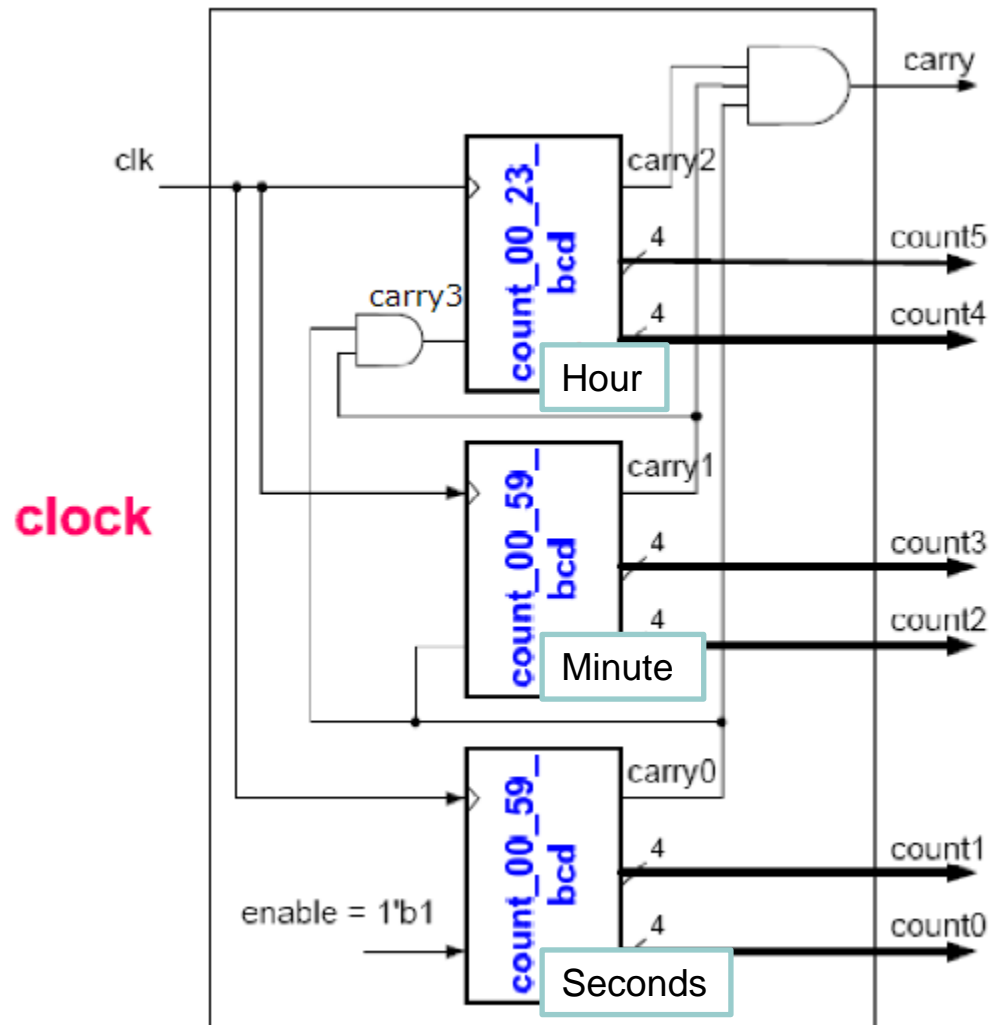


Architecture model for clock_top

clock_top

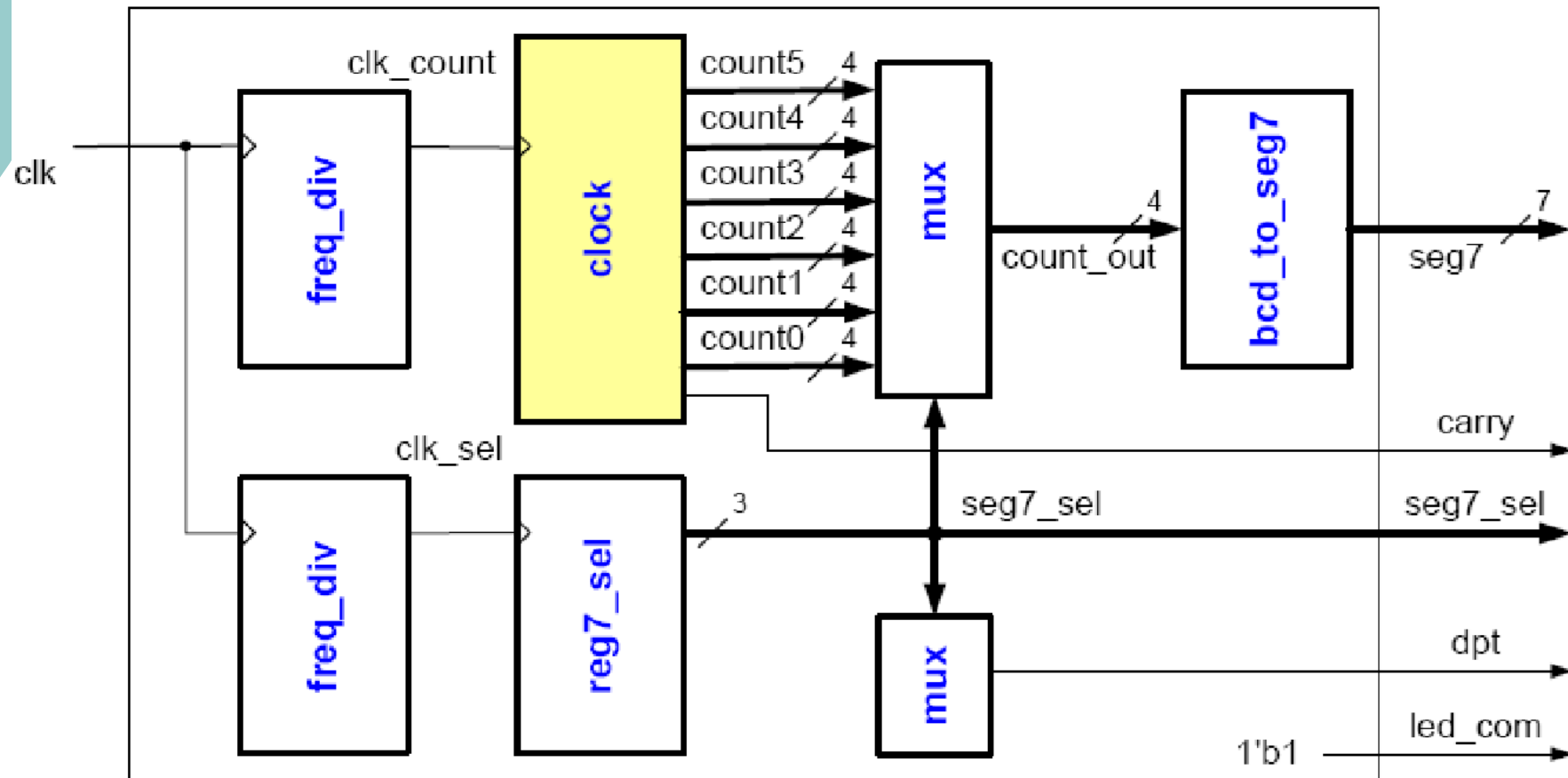

Verilog Code -count_00_59_bcd.v


- **module count_00_59_bcd**(clk, reset, enable, count1, count0, carry);
- **input** clk, reset, enable;
- **output** [3:0] count1, count0;
- **reg**[3:0] count1, count0;
- **output** carry;
- **wire** carry = (count1 == 4'b0101 && count0 == 4'b1001) ? 1 : 0;
- **always@ (posedge clk or posedge reset)begin**
- **if(reset) begin**
- count1 = 4'b0000; // 00
- count0 = 4'b0000;
- **end**



- **else if(enable == 1'b1) begin**
- **if (count1 == 4'b0101 && count0 == 4'b1001) begin// 59**
- **count1 = 4'b0000; // 00**
- **count0 = 4'b0000;**
- **end**
- **else if(count0 == 4'b1001) begin**
- **count0 = 4'b0000;**
- **count1 = count1+ 1'b1;**
- **end**
- **else**
- **count0 = count0+ 1'b1;**
- **end**
- **end**
- **endmodule**

Verilog Code -count_00_23_bcd.v

- **module count_00_23_bcd**(clk, reset, enable, count1, count0, carry);
- **input** clk, reset, enable;
- **output**[3:0] count1, count0;
- **reg**[3:0] count1, count0;
- **output** carry;
- ~~~~~your code~~~~~
- **always@ (posedge clk or posedge reset)begin**
- **if**(reset) **begin**
- ~~~~~your code~~~~~
- **end**

- 
-
- **else if(enable == 1'b1) begin**
 - **if (~~~~~your code~~~~~) begin// 23**
 - ~~~~~your code~~~~~
 - **end**
 - **else if(~~~~~your code~~~~~) begin**
 - ~~~~~your code~~~~~
 - **end**
 - **else**
 - ~~~~~your code~~~~~
 - **end**
 - **end**
 - **endmodule**

Verilog Code -clock.v

- **module clock**(clk, reset, enable, count5, count4, count3, count2, count1, count0, carry);
- **input** clk, reset, enable;
- **output**[3:0]count5, count4, count3, count2, count1, count0;
- **output** carry;
- **wire**[3:0]count5, count4, count3, count2, count1, count0;
- **wire** carry, carry3, carry2, carry1, carry0;
- **assign** carry = *~~your code~~~* ;
- **assign** carry3 = *~~your code~~~* ;
- **count_00_23_bcd**(clk, reset, *~~your code~~~*);
- **count_00_59_bcd**(clk, reset, *~~your code~~~*);
- **count_00_59_bcd**(clk, reset, *~~your code~~~*);
- **endmodule**

Verilog Code -clock_top.v

Main module

- **module clock_top**(clk, reset, enable, seg7_sel, seg7_out, dpt, carry, led_com);
- **input** clk, reset, enable;
- **output**[2:0]seg7_sel;
- **output**[6:0] seg7_out;
- **output** dpt, carry, led_com;
- **wire** clk_count, clk_sel;
- **wire**[3:0] count_out, count5, count4, count3, count2, count1, count0;
- **assign** led_com= 1'b1;
- **assign** count_out= (seg7_sel == 3'b101)? count0 : (seg7_sel == 3'b100)? count1 :
- (seg7_sel == 3'b011)? count2 :
- (seg7_sel == 3'b010)? count3 :
- (seg7_sel == 3'b001)? count4 : count5;

-
- **assign** dpt= (seg7_sel == 3'b101)? 1'b1 :
(seg7_sel == 3'b100)? 1'b0 :
 - (seg7_sel == 3'b011)? 1'b1 :
 - (seg7_sel == 3'b010)? 1'b0 :
 - (seg7_sel == 3'b001)? 1'b1 :1'b0;

 - **freq_div**#(21)(your code);
 - **freq_div**#(15)(your code);
 - **clock**(~~your code~~~);
 - **bcd_to_seg7**(~~your code~~~);
 - **seg7_select**#(?) (~~your code~~~);
 - **endmodule**



Extra Question

- Create a 24-hour clock with accurate reading time.
(Use the 10MHz clock for the seconds)